
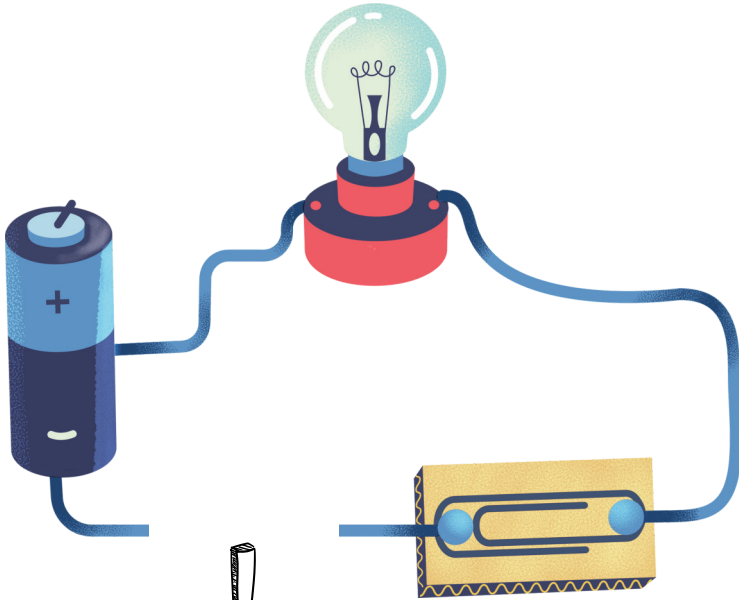


Does it conduct?

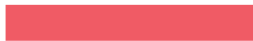


Does it conduct?



Test the conductivity of the materials in the conductivity test kit!



Simple Electric Circuit

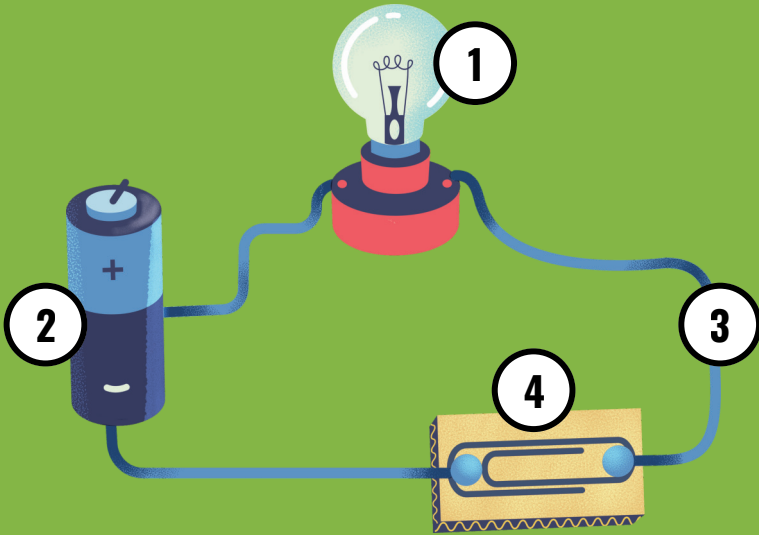

1

It is a receiver that converts electrical energy into light.

2

It is the source that supplies energy to the circuit.

3

It is the connection that conducts electricity.

4

It enables the circuit to be turned on and off.



Write the names of the circuit components in the blanks!